


dce 2019



Digital Systems

Counters and Registers

BK TP.HCM

dce 2019

Introduction

- FFs and logic gates are combined to form various counters and registers.
- Part 1 covers counter principles, various counter circuits, and IC counters.
- Part 2 covers several types of IC registers and shift register counter troubleshooting.

BK TP.HCM

dce 2019


Asynchronous (Ripple) Counters

- Review of four bit counter operation (refer to next slide)
 - Clock is applied only to FF A. J and K are high in all FFs to toggle on every clock pulse.
 - Output of FF A is CLK of FF B and so forth.
 - FF outputs D, C, B, and A are a 4 bit binary number with D as the MSB.
 - After the negative transition of the 15th clock pulse the counter recycles to 0000.
- This is an **asynchronous** counter because state is not changed in exact synchronism with the clock.


BK TP.HCM

dce 2019

Four-bit asynchronous (ripple) counter

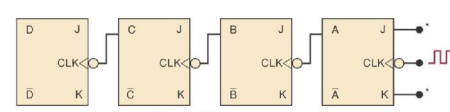

*All J and K inputs assumed to be 1.

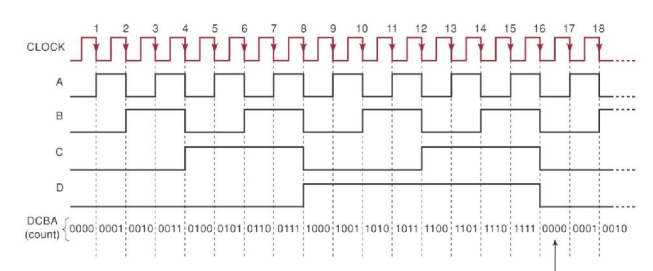

DCBA (count) 0000; 0001; 0010; 0011; 0100; 0101; 0110; 0111; 1000; 1001; 1010; 1011; 1100; 1101; 1110; 1111; 0000; 0001; 0010


Recycle to 0000

□ MOD = the number of states

BK TP.HCM

Frequency division

 
- The output frequency of each FF = the clock frequency of input / 2.
- The output frequency of the last FF = the clock frequency / MOD.



Propagation Delay in Ripple Counters


- Ripple counters are simple, but the cumulative propagation delay can cause problems at high frequencies.
- For proper operation the following apply:
 - $T_{\text{clock}} \geq N \times t_{pd}$
 - $F_{\text{max}} = 1/(N \times t_{pd})$

Ripple Counter Propagation Delay

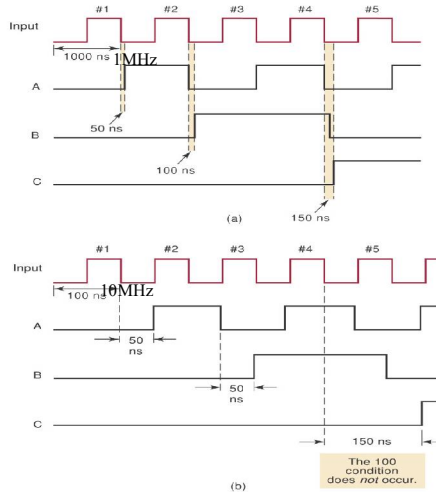Counters with MOD Number $< 2^N$


- Find the smallest MOD required so that 2^N is less than or equal to the requirement.
- Connect a NAND gate to the asynchronous CLEAR inputs of all FFs.
- Determine which FFs are HIGH at the desired count and connect the outputs of these FFs to the NAND gate inputs.

 State transition diagram for the MOD-6 counter



MOD-6 Counter

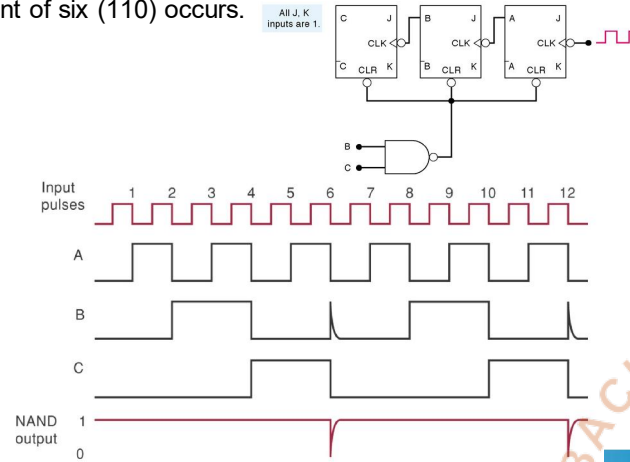MOD-6 counter produced by clearing a MOD-8 counter when a count of six (110) occurs.



Counters with MOD Number $< 2^N$


- General Procedures Counter Design
 - Find the smallest number of FF
 - Connect a NAND gate to the Asynchronous CLEAR inputs of all the FFs
 - Determine which FFs will be in the HIGH state at a count = X; then connect the normal outputs of these FFs to the NAND gate inputs

Decade counters/BCD counters

- Decade counters/BCD counters
 - A decade counter is any counter with 10 distinct states, regardless of the sequence. Any MOD-10 counter is a decade counter.
 - A BCD counter is a decade counter that counts from binary 0000 to 1001.
- Decade counters are widely used for counting events and displaying results in decimal form.

Asynchronous Down Counter

 - All of the counters we have looked were up counters.
- Down counter counts number downward e.g: 111 \rightarrow 000




Asynchronous Down Counter

- Each FF, except the first must toggle when the preceding FF goes from LOW to HIGH
- If the FFs have CLK inputs that respond to negative transition (HIGH to LOW), then an inverter can be placed in front of each CLK input; however the same effect can be accomplished by driving each FF CLK input from the inverted output of the preceding FF.
- Input pulses are applied to A. The A' output serves as the CLK input for B; the B' output serves as the CLK input for the C.
- The waveforms at A, B and C show that B toggles whenever A goes LOW to HIGH and C toggles whenever B goes LOW to HIGH.




13

Asynchronous Down Counter

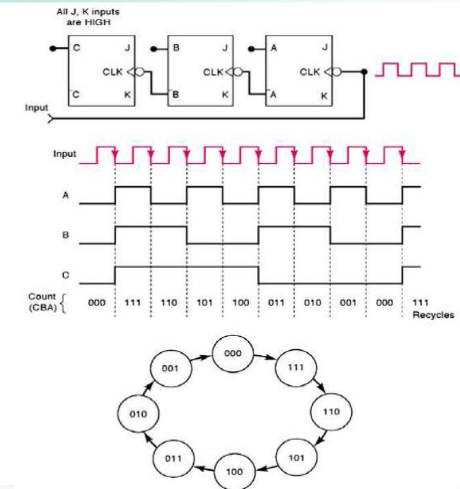

14


IC Asynchronous counter

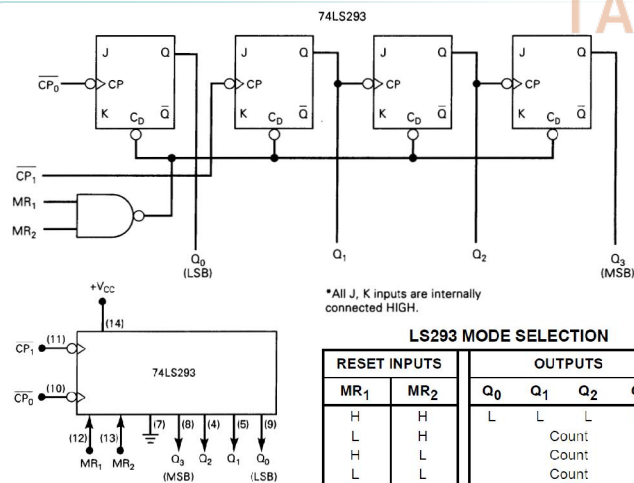

15

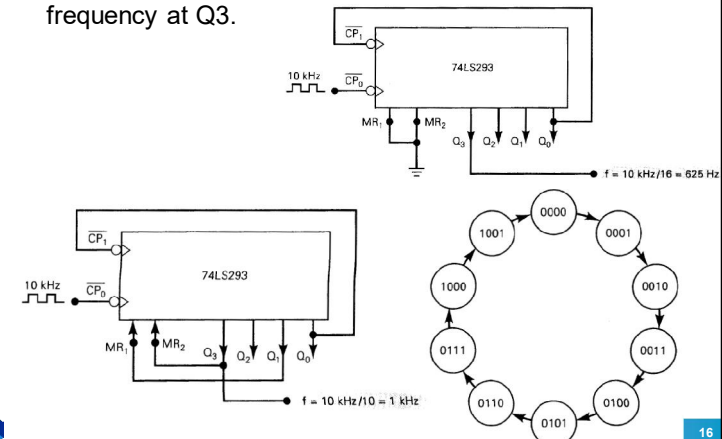Example

- Show how to wire the 74LS293 as a MOD-16, MOD-10 counter with a 10-kHz clock input. Determine the frequency at Q₃.



16

Example

- Show how to wire the 74LS293 as a MOD-14, MOD-60, counter with a 10-kHz clock input.




17

Synchronous (Parallel) Counters

- All FFs are triggered by CLK **simultaneously**
- Mod-16 counter.
 - Each FF has J and K inputs connected so they are **HIGH only when the outputs of all lower-order FFs are HIGH**.
 - **The total propagation delay will be the same for any number of FFs.**
- Synchronous counters can operate at much higher frequencies than asynchronous counters.

Count	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
0	0	0	0	0

 

18

Synchronous (Parallel) Counters

- **Circuit Operation**
 - On a given NGT of the clock, only those FFs that are supposed to toggle on that NGT should have J=K=1 when that NGT occurs.
 - FF A must change states at each NGT. Its J and K inputs are permanently HIGH so that it will toggle on each NGT of the CLK input.
 - FF B must change states on each NGT that occurs while A=1.
 - FF C must change states on each NGT that occurs while A=B=1
 - FF D must change states on each NGT that occurs while A=B=C=1



19

Synchronous (Parallel) Counters


- Each FF should have its J&K inputs connected such that they are HIGH only when the outputs of all lower-order FFs are in the HIGH state.
- Advantages over asynchronous:
 1. FFs will change states simultaneously; synchronized to the NGTs of the input clock pulses.
 2. Propagation delays of the FFs do not add together to produce the overall delay.
 3. The total response time is the time it takes one FF to toggle plus the time for the new logic levels to propagate through a single AND gate to reach the J, K inputs.
- **total delay = FF *tpd* + AND gate *tpd***




20

Counters for $\text{MOD} < 2^N$

 MOD-14 counter
resets when count
14 is reached.




 MOD-10 (decade)
counter. Resets
when count 10 is
reached.




Example: MOD-60 Counter

Resets when count 60 is reached.

 


Synchronous, MOD-16, down counter

 

Synchronous Down and Up/Down Counters

 
- The synchronous counter can be converted to a down counter by using the inverted FF outputs to drive the JK inputs.



MOD-8 synchronous up/down counter

The counter counts up when the control input Up/Down = 1;
it counts down when the control input Up/Down = 0.

MOD-8 synchronous up/down counter

 


The counter counts up when the control input Up/Down = 1; A and B signals are passed
it counts down when the control input Up/Down = 0; inverted A and B signals are passed


Presettable Counters

- A presettable counter can be set to any desired starting point either asynchronously or synchronously.
- The preset operation is also called parallel loading the counter.

 Synchronous counter with asynchronous parallel load



IC Synchronous Counters

 

Part Number	Modulus
74ALS160	10
74ALS161	16
74ALS162	10
74ALS163	16

(b)

74ALS160-74ALS163 Function Table						
CLR	LOAD	ENT	ENP	CLK	Function	Part Numbers
L	X	X	X	X	Asynch. Clear	74ALS160 & 74ALS161
L	X	X	X	↑	Synchr. Clear	74ALS162 & 74ALS163
H	L	X	X	↑	Synchr. Load	All
H	H	H	H	↑	Count up	All
H	H	L	X	X	No change	All
H	H	X	L	X	No change	All

(c)

- 4 FFs,

- PGT at the CLK input,

- The counter can be preset to any value (applied to the A, B, C, and D inputs) by applying an active-low LOAD input.

Synchronous Counter Example

74HC163

- start counting at t1
- synchronous** clear at t2
- synchronous** load at t3
- stop counting at t4 (ENP low)
- no counting at t5 (ENT low)
- resume counting at t6
- terminal state sets RCO (ripple carry out) high automatic reset at t7

Synchronous Counter Example

74HC160

- start counting at t1
- asynchronous** clear at t2
- asynchronous** clear at t3
- stop counting at t4 (ENP low)
- synchronous load at t5
- stop counting at t6 (ENT low)
- continue counting at t7
- terminal state of 1001 sets RCO
- stop counting at t8 (ENP)
- RCO goes low at t9 due to low ENT (ENP does not affect RCO)

74ALS190-75ALS191 series synchronous counters (up/down)

74ALS190-74ALS191

Part Number	Modulus
74ALS190	10
74ALS191	16

(b)

LOAD	CTEN	D/U	CLK	Function
L	X	X	X	Asynch. Load
H	L	L	↑	Count up
H	L	H	↑	Count down
H	H	X	X	No change

(c)

MOD-10 Counter

74ALS190-74ALS191 Function Table


LOAD	CTEN	D/U	CLK	Function
L	X	X	X	Asynch. Load
H	L	L	↑	Count up
H	L	H	↑	Count down
H	H	X	X	No change

Synchronous Counter Example

Using 74ALS163 (syn load) and 74ALS191 (async load) MOD-16 counters for other MODs


Synchronous load
0001-1100
mod-12 counter

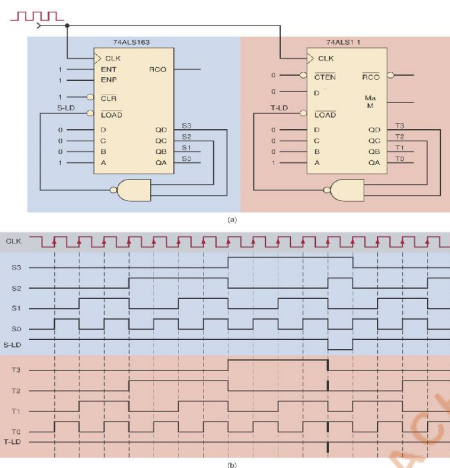asynchronous load
0001-1011
mod-11 counter (in 1100
state for a short period of time)



33

Extending Maximum Counting Range

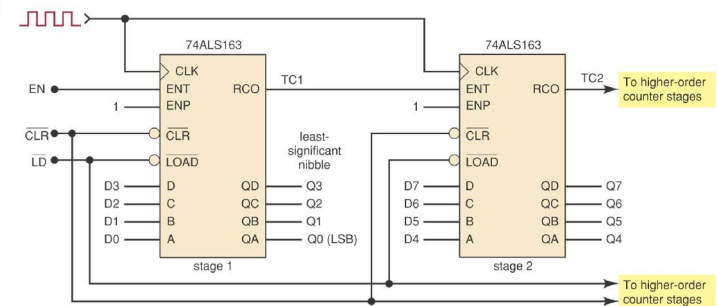

34


Decoding a Counter

- Decoding is the conversion of a binary output to a decimal value.
- The active high decoder could be used to light an LED representing each decimal number 0 to 7.
- Active low decoding is obtained by replacing the AND gates with NAND gates.


35

Decoding a Counter

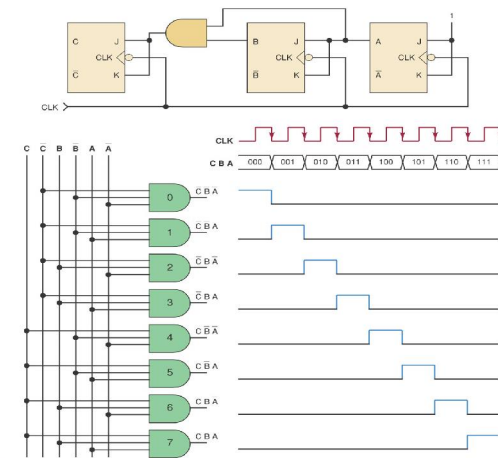Using AND Gates to Decode a MOD-8 Counter (produce pulse at specific count)



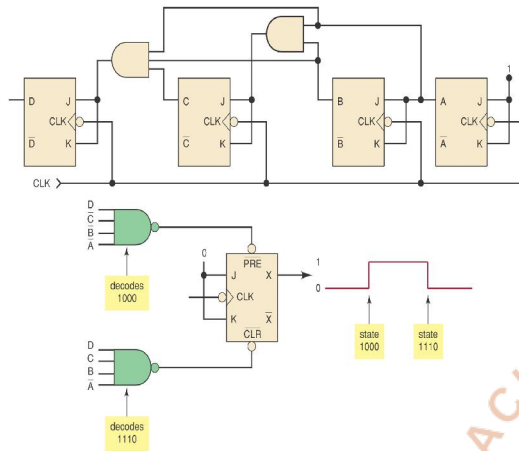
Circuit to Make X High Between Counts of 8 and 14
(sets FF at count 8, then clears at count 14)



3

- Example of a synchronous up counter.
 - The control inputs are as follows: $J_C = A \cdot B$, $K_C = C$, $J_B = K_B = A$, $J_A = K_A = \overline{C}$

38

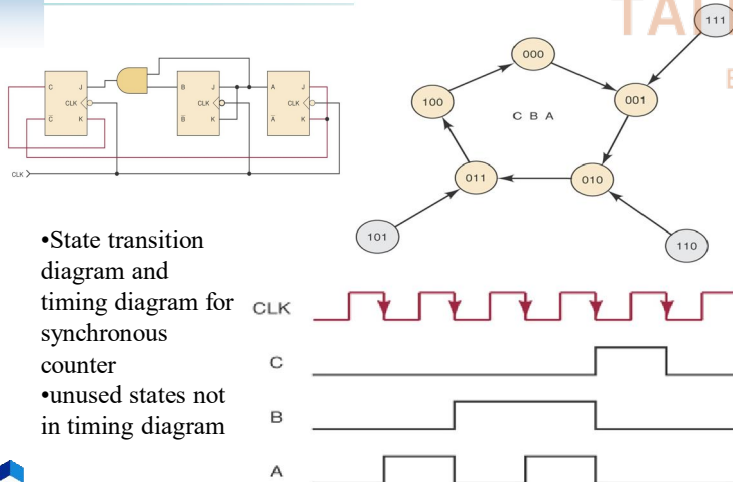


35

- Determine desired number of bits and desired counting sequence
- Draw the state transition diagram showing all possible states
- Use the diagram to create a table listing all PRESENT states and their NEXT states
- Add a column for each JK input (or other inputs). Indicate the level required at each J and K in order to produce transition to the NEXT state.
- Design the logic circuits to generate levels required at each JK input.
- Implement the final expressions.

40

Choose a type of FF – JK in this example

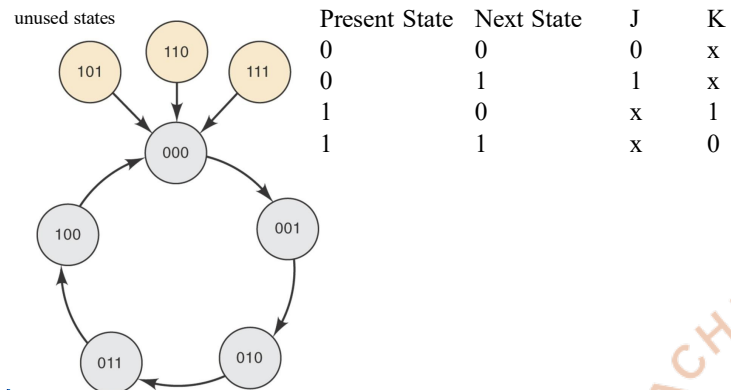State transition diagram for the synchronous counter design



State table of counter example

JK Flip-Flop excitation table	Present State	Next State	J	K
0	0	0	0	x
0	1	1	1	x
1	0	0	x	1
1	1	1	x	0

	PRESENT State			NEXT State								
	C	B	A	C	B	A	J _C	K _C	J _B	K _B	J _A	K _A
Line 1	0	0	0	0	0	1	0	x	0	x	1	x
2	0	0	1	0	1	0	0	x	1	x	x	1
3	0	1	0	0	1	1	0	x	x	0	1	x
4	0	1	1	1	0	0	1	x	x	1	x	1
5	1	0	0	0	0	0	x	1	0	x	0	x
6	1	0	1	0	0	0	x	1	0	x	x	1
7	1	1	0	0	0	0	x	1	x	1	0	x
8	1	1	1	0	0	0	x	1	x	1	x	1

K maps for the J and K logic circuits

K map used to obtain the simplified expression for J_A ; from the state table

	PRESENT State			NEXT State								
	C	B	A	C	B	A	J _C	K _C	J _B	K _B	J _A	K _A
Line 1	0	0	0	0	0	1	0	x	0	x	1	x
2	0	0	1	0	1	0	0	x	1	x	x	1
3	0	1	0	0	1	1	0	x	x	0	1	x
4	0	1	1	1	0	0	1	x	x	1	x	1
5	1	0	0	0	0	0	x	1	0	x	0	x
6	1	0	1	0	0	0	x	1	0	x	x	1
7	1	1	0	0	0	0	x	1	x	1	0	x
8	1	1	1	0	0	0	x	1	x	1	x	1

	\bar{A}	A
$\bar{C} \bar{B}$	1	X
$\bar{C} B$	1	X
$C \bar{B}$	0	X
$C B$	0	X

$$J_A = \bar{C}$$

(b)

K maps for the J and K logic circuits

	\bar{A}	A
$\bar{C} \bar{B}$	0	1
$\bar{C} B$	X	X
$C \bar{B}$	X	X
$C B$	0	0

$J_B = \bar{C} A$

	\bar{A}	A
$\bar{C} \bar{B}$	X	X
$\bar{C} B$	0	1
$C \bar{B}$	1	1
$C B$	X	X

$K_B = C + A$

	\bar{A}	A
$\bar{C} \bar{B}$	0	0
$\bar{C} B$	0	1
$C \bar{B}$	X	X
$C B$	X	X

$J_C = B A$

	\bar{A}	A
$\bar{C} \bar{B}$	X	X
$\bar{C} B$	X	X
$C \bar{B}$	1	1
$C B$	1	1

$K_C = 1$

(a)

(b)

	PRESENT State			NEXT State								
	C	B	A	C	B	A	J _C	K _C	J _B	K _B	J _A	K _A
Line 1	0	0	0	0	0	1	0	x	0	x	1	x
2	0	0	1	0	1	0	0	x	1	x	x	1
3	0	1	0	0	1	1	0	x	x	0	1	x
4	0	1	1	1	0	0	1	x	x	1	x	1
5	1	0	0	0	0	0	x	1	0	x	0	x
6	1	0	1	0	0	0	x	1	0	x	x	1
7	1	1	0	0	0	0	x	1	x	1	0	x
8	1	1	1	0	0	0	x	1	x	1	x	1

State Table for Example: MOD-5 Counter Using D-type Flip-Flops

PRESENT State			NEXT State			Control Inputs		
C	B	A	C	B	A	D _C	D _B	D _A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

K maps for Outputs - MOD-5 D-flip-flop counter

$\bar{C}\bar{B}$	\bar{A}	A
0	0	0
0	1	0
1	0	0
1	1	0

$$D_C = \bar{C}BA$$

$\bar{C}\bar{B}$	\bar{A}	A
0	0	1
0	1	0
1	0	0
1	1	0


$$D_B = \bar{C}\bar{B}A + \bar{C}B\bar{A}$$

$\bar{C}\bar{B}$	\bar{A}	A
0	0	1
0	1	0
1	0	0
1	1	0

$$D_A = \bar{C}\bar{A}$$

PRESENT State			NEXT State			Control Inputs		
C	B	A	C	B	A	D _C	D _B	D _A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

 Implementation of MOD-5, D flip-flop design




Integrated-Circuit Registers

- Registers can be classified by the way data is entered for storage, and by the way data is outputted from the register.
 - Parallel in/parallel out (PIPO)
 - Serial in/serial out (SISO)
 - Parallel in/serial out (PISO)
 - Serial in/parallel out (SIPO)

PISO – The 74ALS165/74HC165

 - 8 bit register
 - Serial data entry via D_S
 - Asynchronous parallel data entry P_0 through P_7
 - Only the outputs of Q_7 are accessible
- CP is clock input for shifting
- Clock inhibit input
- Shift load input



Function Table


Inputs			Operation
SH/LD	CP	CP INH	
L	X	X	Parallel load
H	H	X	No change
H	X	H	No change
H	f	L	Shifting
H	L	f	Shifting

H = high level
L = low level
X = immaterial
f = PGT

(b)



74HC165 PISO Waveforms

 $D_S = 0$, $CP\ INH = 0$, Output values for given inputs ($P_0=P_7$)



SIPO – The 74ALS164/74HC164

 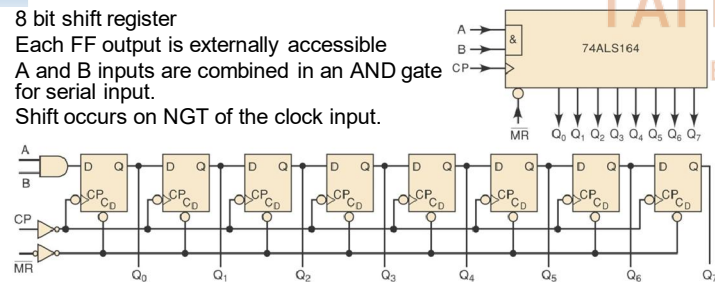- 8 bit shift register
- Each FF output is externally accessible
- A and B inputs are combined in an AND gate for serial input.
- Shift occurs on NGT of the clock input.



Input pulse number

Input pulse number	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇
0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
2	1	1	0	0	0	0	0	0
3	1	1	1	0	0	0	0	0
4	1	1	1	1	0	0	0	0
5	1	1	1	1	1	0	0	0
6	1	1	1	1	1	1	0	0
7	1	1	1	1	1	1	1	0
8	1	1	1	1	1	1	1	1

Recycles

Temporary state

Other similar devices

- 74194/ASL194/HC194
 - 4 bit bi-directional universal shift register
 - Performs shift left, shift right, parallel in and parallel out.
- 74373/ALS373/HC373/HCT373
 - 8 bit PIPO with 8 D latches
 - Tristate outputs
- 74374/ALS374/HC374
 - 8 bit PIPO with 8 edge triggered D FFs, Tristate outputs



Shift Register Counters

- Ring Counter
 - Last FF shifts its value to first FF
 - Uses D-type FFs (JK FFs can also be used)
- Must start with only one FF in the 1 state and all others in the 0 state.




57

Four-bit Ring Counter

  



Q ₃	Q ₂	Q ₁	Q ₀	CLOCK pulse
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7
-	-	-	-	-
-	-	-	-	-

 


58

MOD-6 Johnson counter

  - Johnson counter
 - Also called a twisted ring counter
 - Same as ring counter but the inverted output of the last FF is connected to input of the first FF



Q ₂	Q ₁	Q ₀	CLOCK pulse
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
-	-	-	-
-	-	-	-

 

59